



EE115 Analog Circuits

模拟电路

Dr. Hao Ren 任豪

Office: SIST Bldg 3-328


renhao@shanghaitech.edu.cn

Outline



- Building blocks of IC amplifier
- SEDTRA/SMITH book page 525-556;

Review: Current mirror

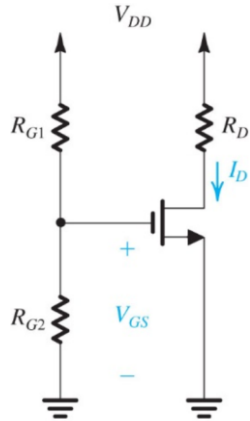


- Neglecting channel length modulation



$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_1 (V_{GS} - V_{tn})^2$$

$$I_O = I_{D2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_2 (V_{GS} - V_{tn})^2$$
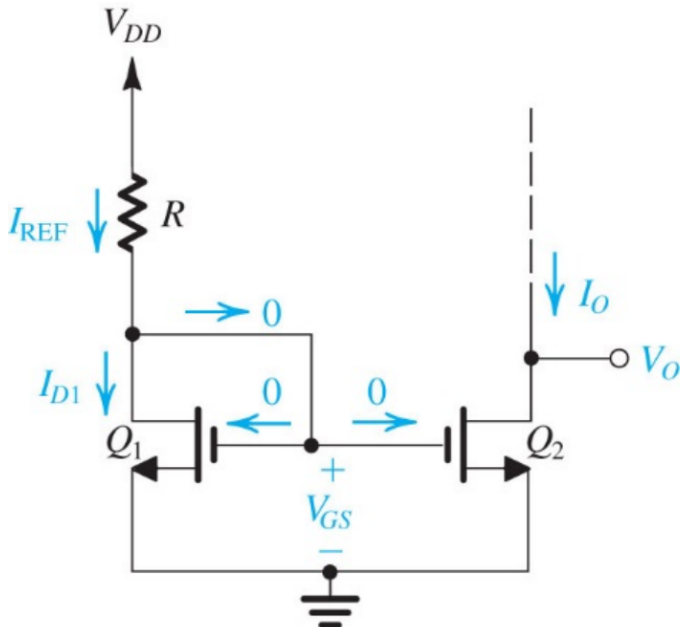
$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$



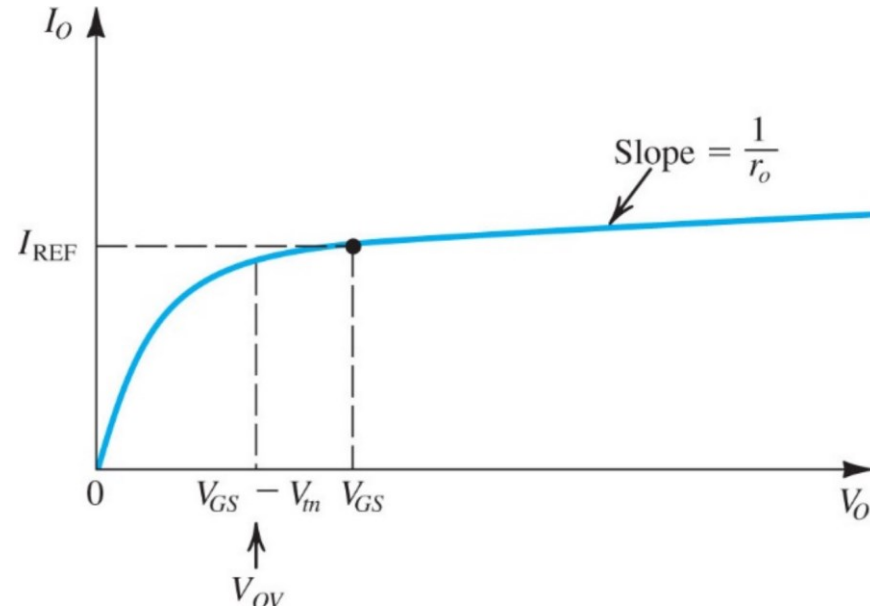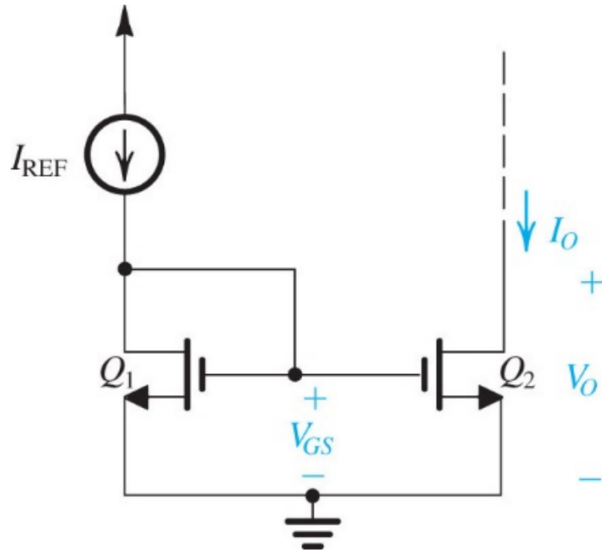Review: Current Mirrors with reference source





- Neglecting channel length modulation

$$\frac{I_O}{I_{\text{REF}}} = \frac{(W/L)_2}{(W/L)_1}$$

- If considering channel length modulation

$$I_O = \frac{(W/L)_2}{(W/L)_1} I_{\text{REF}} \left(1 + \frac{V_O - V_{GS}}{V_{A2}} \right)$$

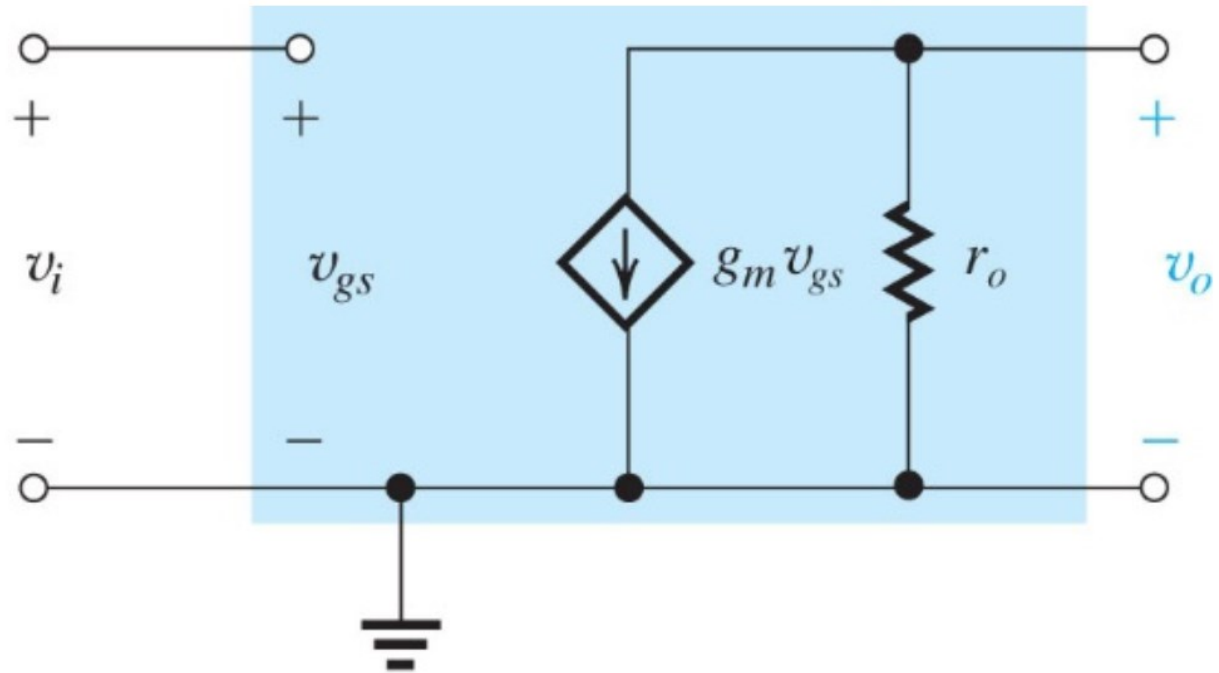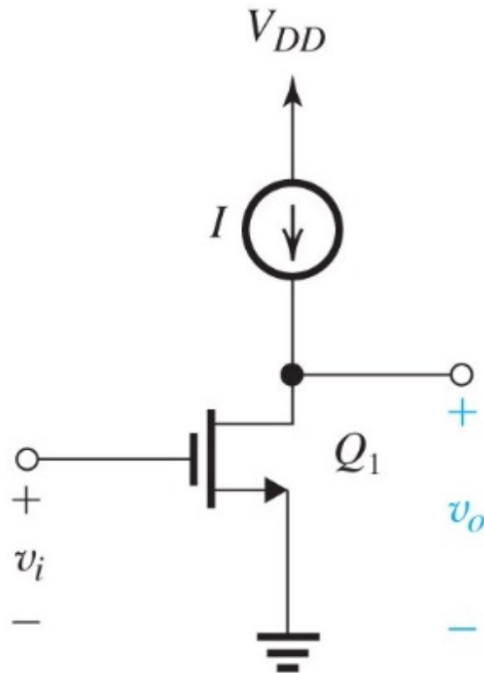Review: Basic Gain Cells with Ideal Current Source Load



$$g_m = \frac{I_D}{V_{OV}/2}$$

$$g_m = \sqrt{2k'_n} \sqrt{W/L} \sqrt{I_D}$$

$$r_o = \frac{V_A}{I_D} = \frac{V'_A L}{I_D}$$


$$A_0 = \frac{V_A}{V_{OV}/2} = \frac{2V'_A L}{V_{OV}}$$

$$R_{in} = \infty$$

Intrinsic gain: $A_{vo} = -g_m r_o$

$$R_o = r_o$$

Review: The Intrinsic Gain $g_m r_o$

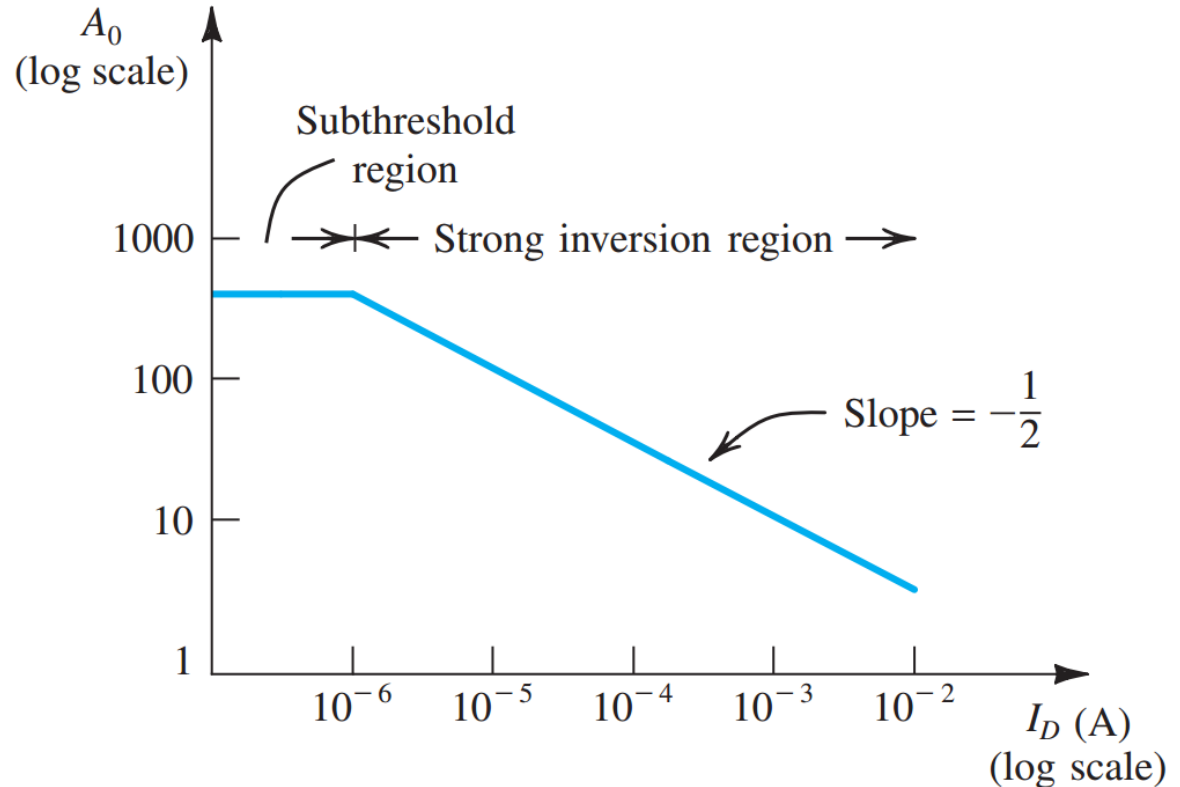

• MOSFET



$$A_0 = \frac{V'_A \sqrt{2(\mu_n C_{ox})(WL)}}{\sqrt{I_D}}$$

$$g_m = \sqrt{2k'_n} \sqrt{W/L} \sqrt{I_D} \quad r_o = \frac{|V_A|}{I_D}$$

$$V_{OV} = \sqrt{2I_D / (k'_n(W/L))}$$

Smaller current gives higher gain, but paid by smaller g_m and bandwidth.

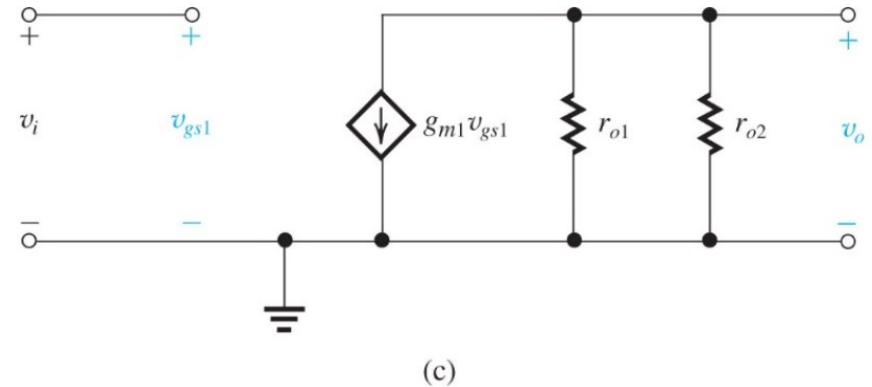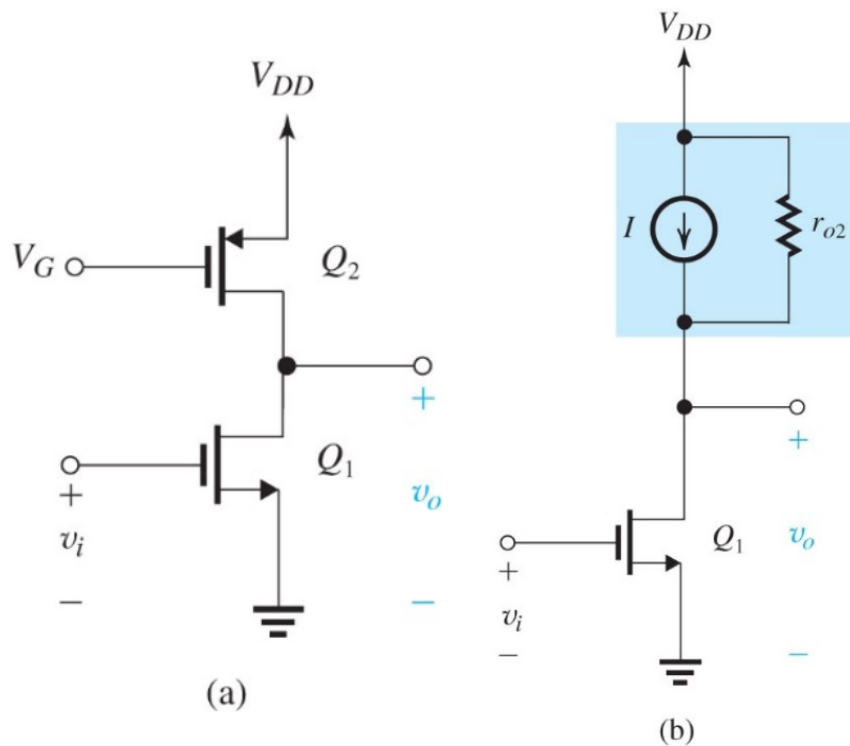Review: Output Resistance of Current Source Load







$$r_{o2} = \frac{|V_{A2}|}{I}$$



$$I = \frac{1}{2}(\mu_p C_{ox}) \left(\frac{W}{L} \right)_2 [V_{DD} - V_G - |V_{tp}|]^2$$

$$A_v \equiv \frac{v_o}{v_i} = -g_{m1}(r_{o1} \parallel r_{o2})$$

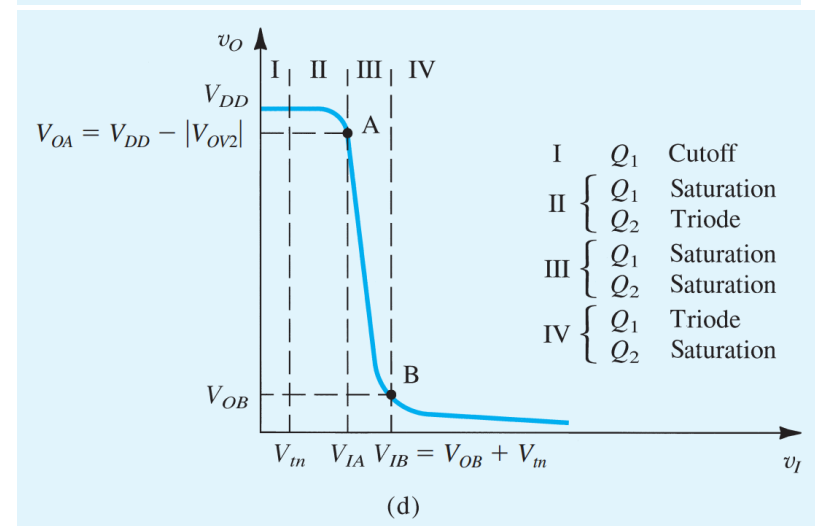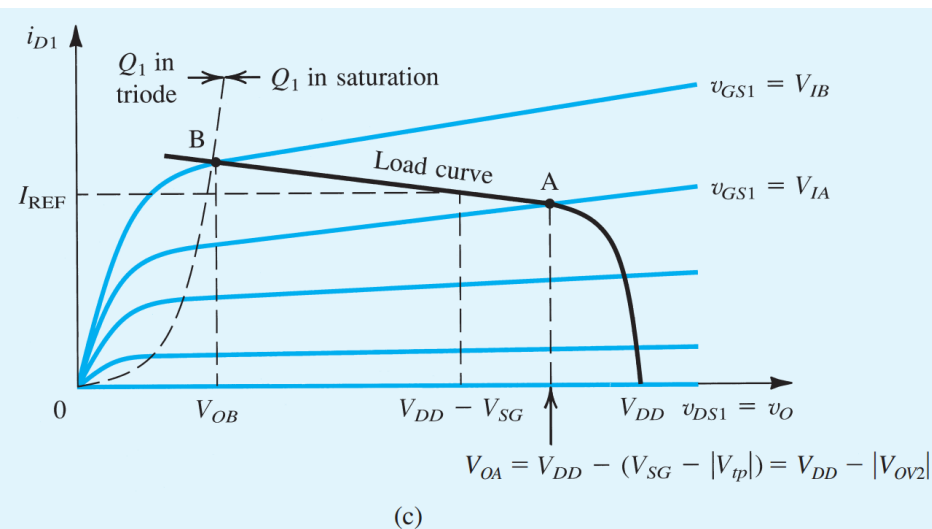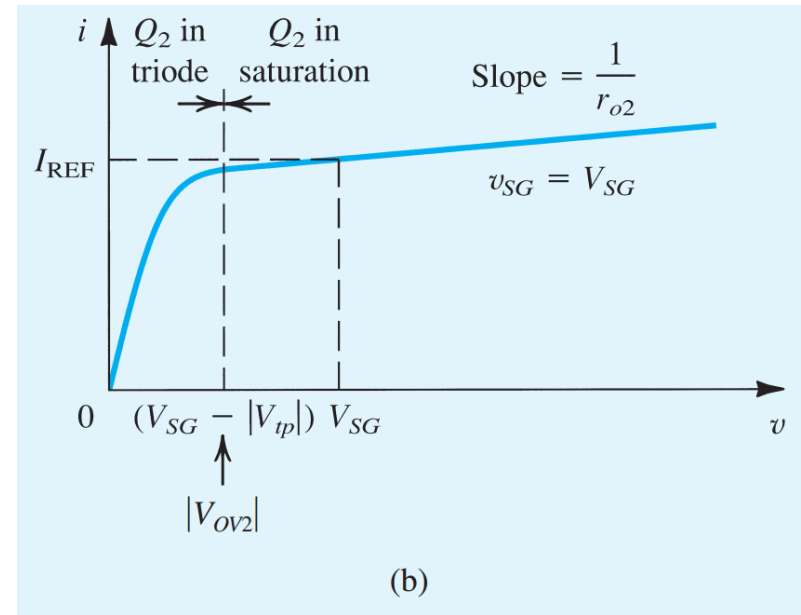
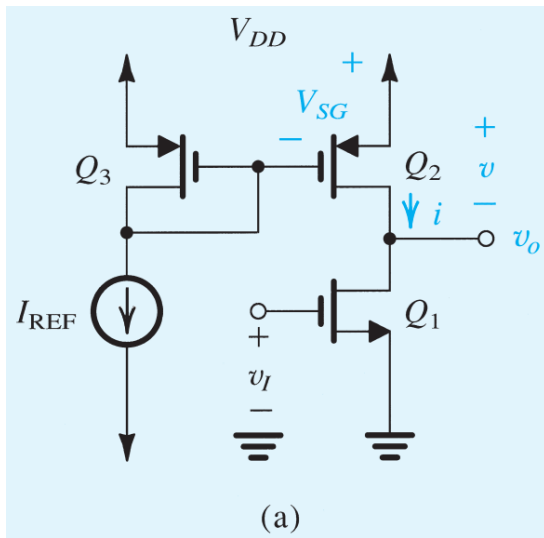
Graphical Solution of Voltage Transfer Curve



How To Increase Voltage Gain?

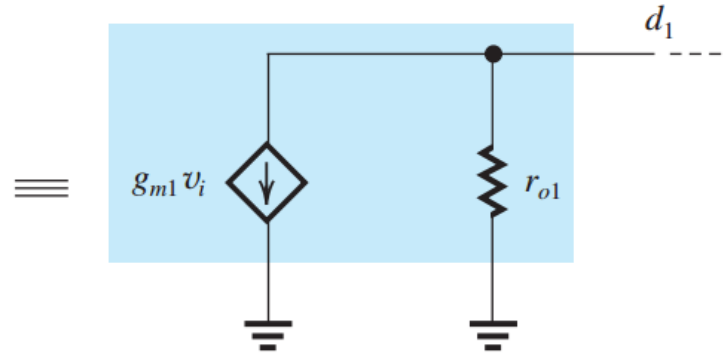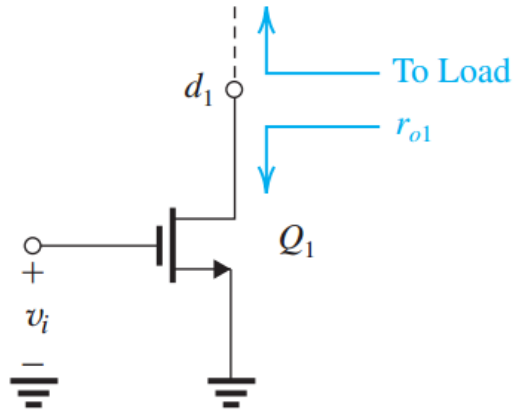


(a)

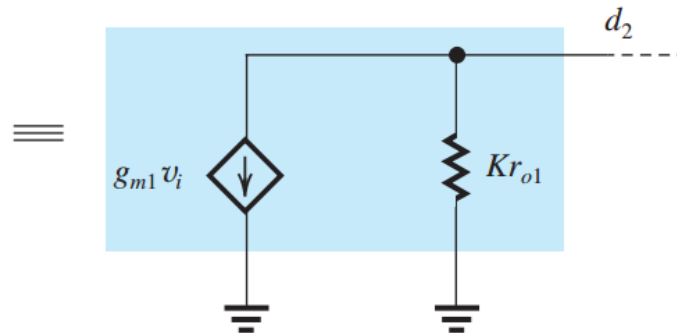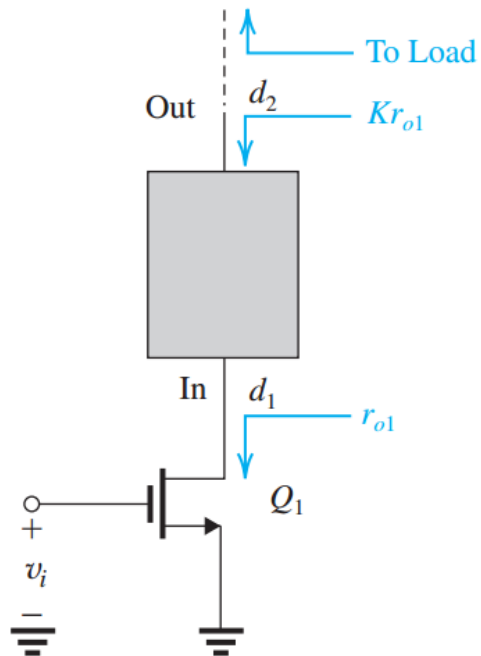

(b)

Continued 1

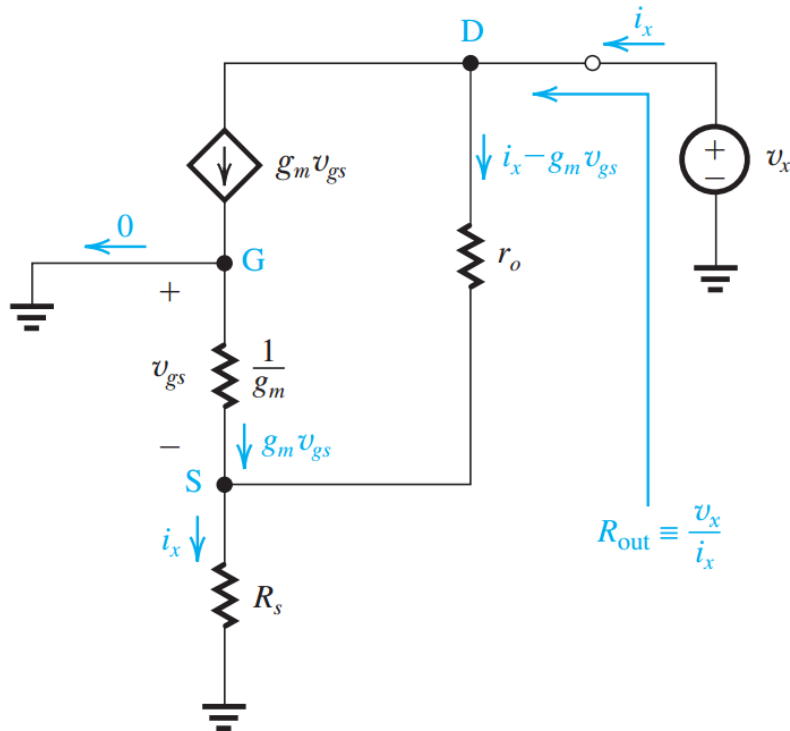

$$v_x = (i_x - g_m v_{gs})r_o + i_x R_s$$

$$v_{gs} = -i_x R_s$$


$$R_{\text{out}} = r_o + R_s + g_m r_o R_s$$

$$= r_o + (1 + g_m r_o)R_s$$

$$\simeq (g_m r_o)R_s$$

The source impedance is transformed to the output by multiplying the intrinsic gain.

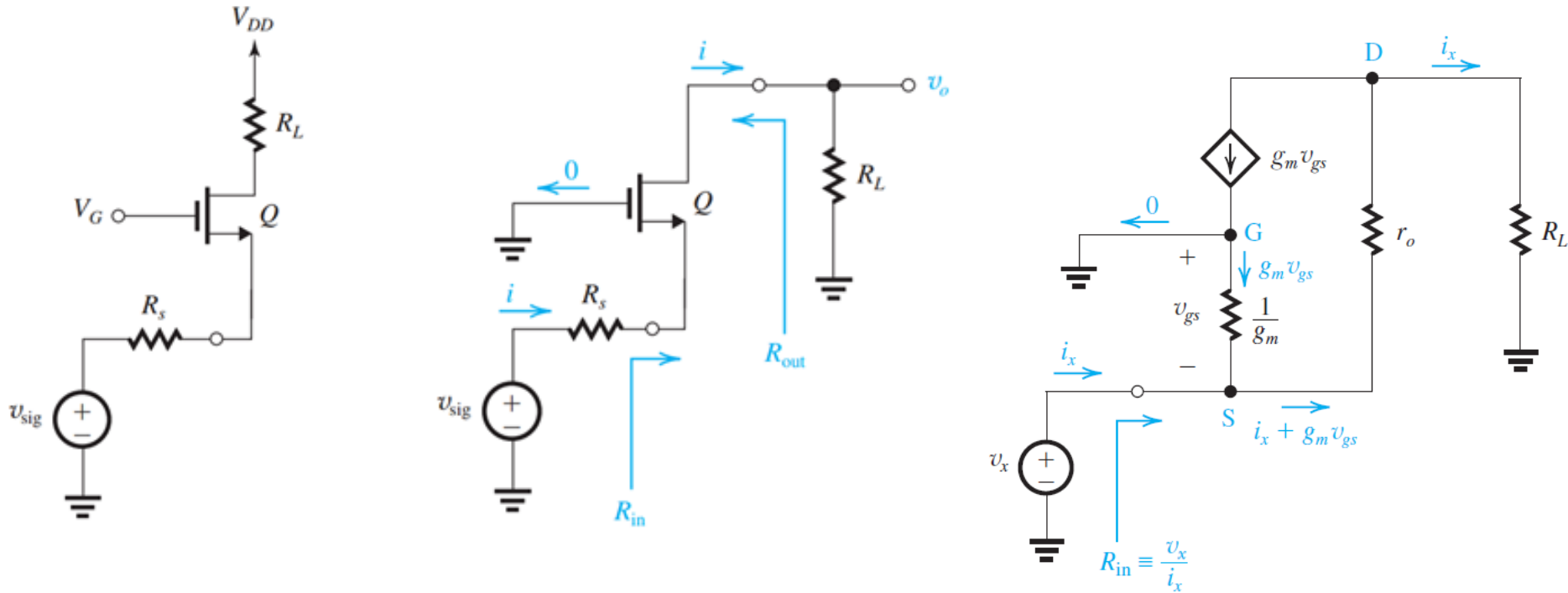Impedance Transformation of Common Gate Amplifier




$$v_x = (i_x + g_m v_{gs}) r_o + i_x R_L$$

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o} \simeq \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

The load impedance is transformed to the input by dividing by the intrinsic gain.


Continued 2

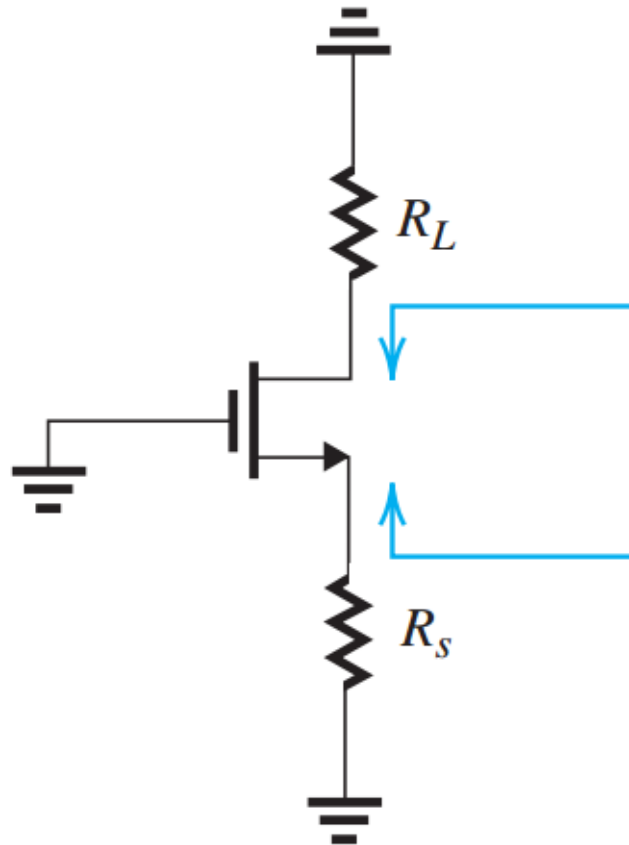

$$R_{out} = r_o + R_S + g_m r_o R_S \\ \simeq r_o + (g_m r_o) R_S$$

$$R_{in} = \frac{r_o + R_L}{1 + g_m r_o} \\ \simeq \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

MOS Cascode Amplifier

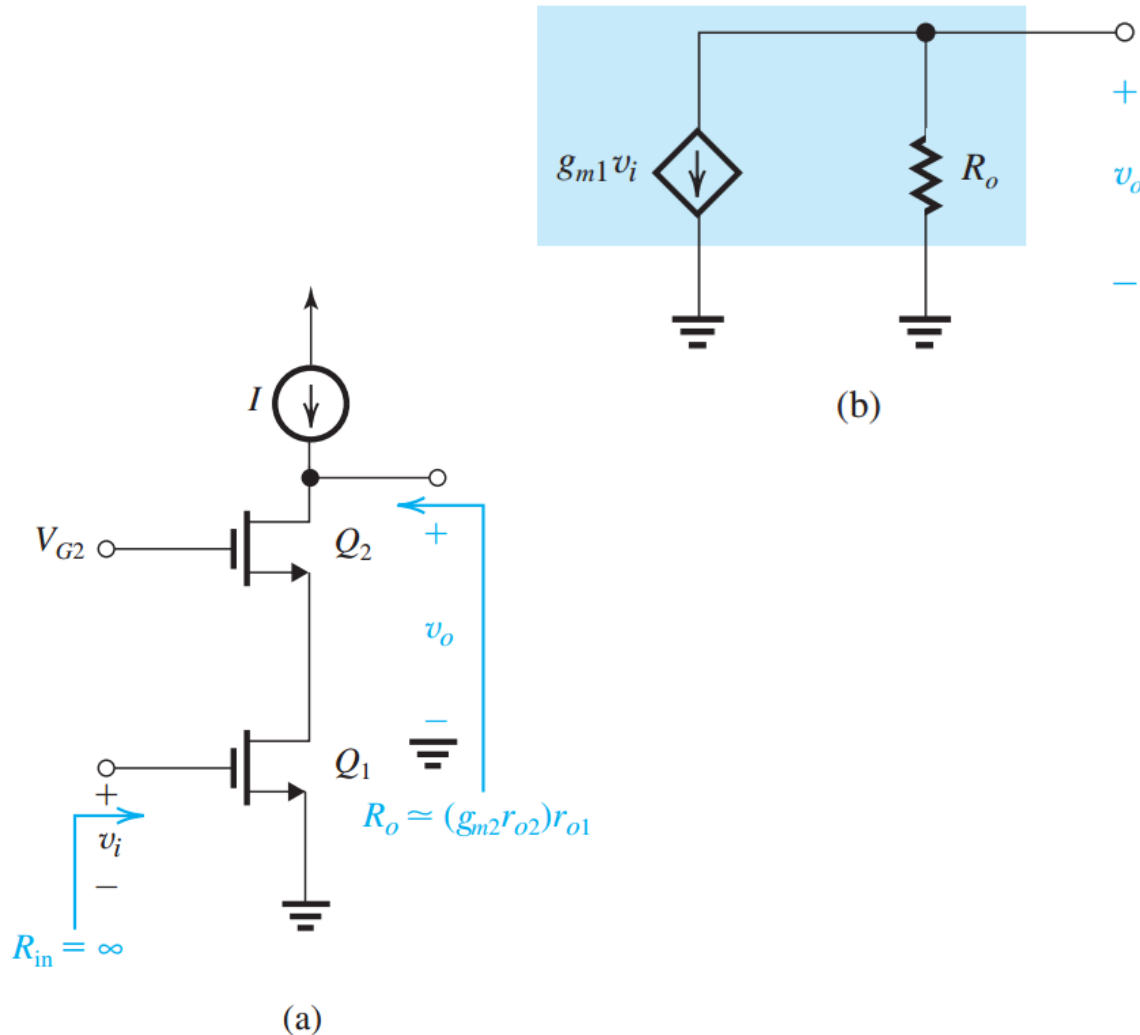



$$A_{vo} \equiv \frac{v_o}{v_i} = -g_{m1} R_o$$

$$R_o \simeq (g_{m2} r_{o2}) r_{o1}$$

$$A_{vo} = -(g_{m1} r_{o1})(g_{m2} r_{o2})$$


$$\begin{aligned} A_{vo} &= -(g_m r_o)^2 \\ &= -A_0^2 \end{aligned}$$

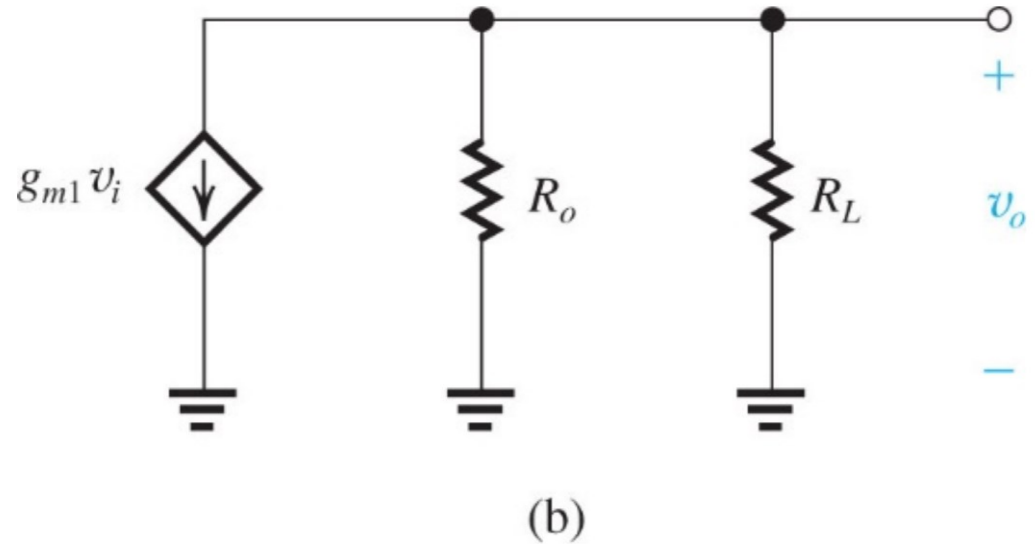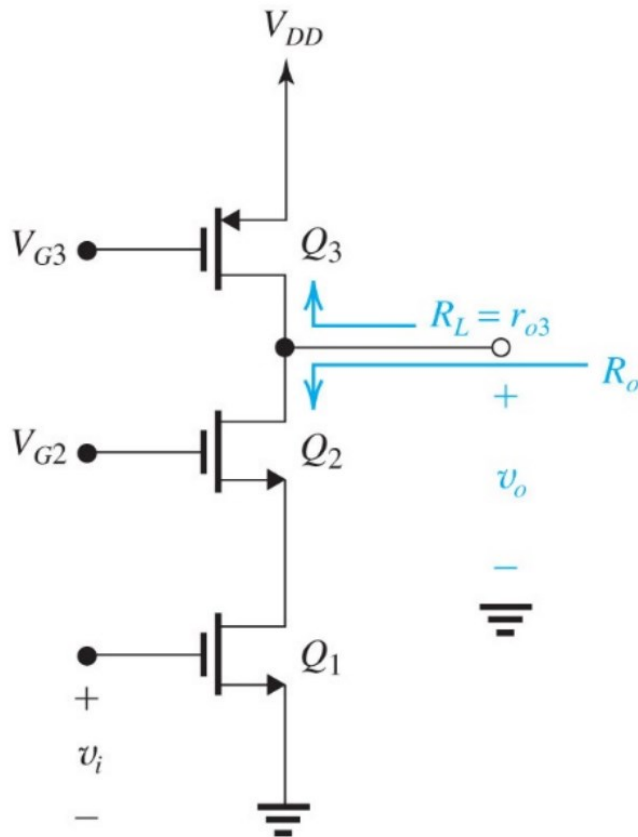Cascode Amplifier with Simple Active Load




$$\begin{aligned}
 A_v &= -g_{m1}(R_o \parallel R_L) \\
 &= -g_{m1}(g_{m2}r_{o2}r_{o1} \parallel r_{o3}) \\
 &\simeq -g_{m1}r_{o3}
 \end{aligned}$$

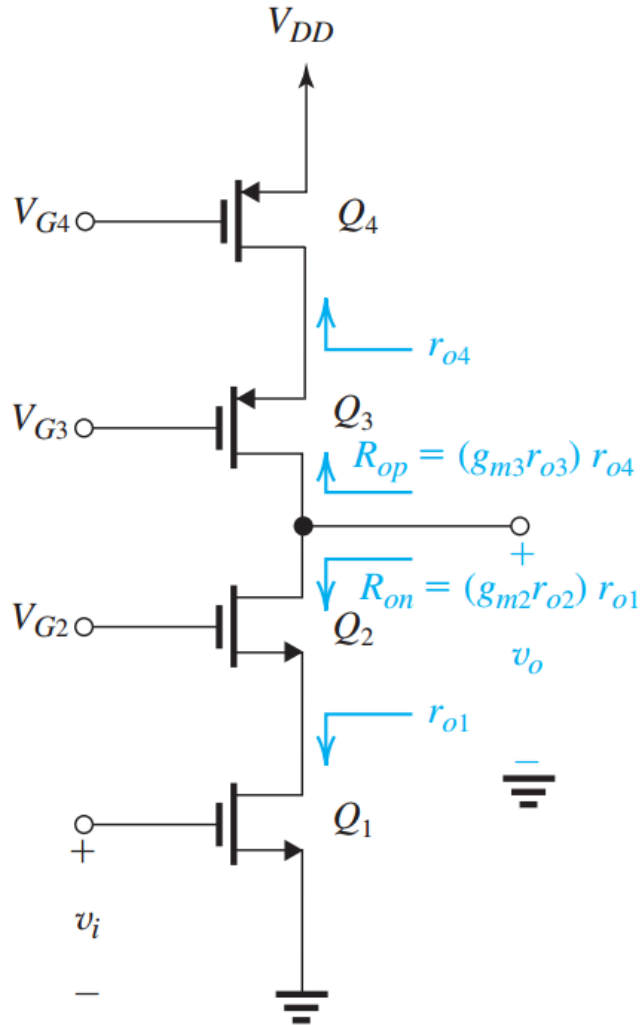Cascode Amplifier with Cascode Current-Source Load



(a)

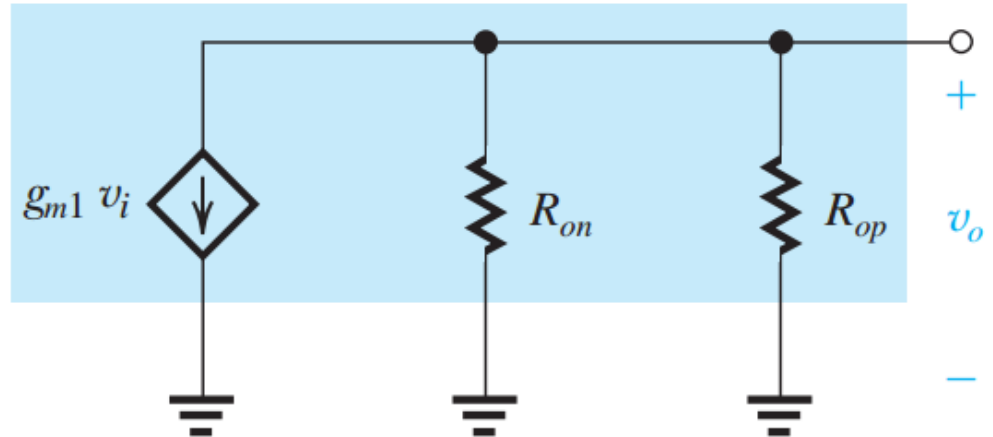

(b)

$$A_v = -g_{m1} \{ [(g_{m2} r_{o2}) r_{o1}] \parallel [(g_{m3} r_{o3}) r_{o4}] \}$$

$$A_v = -\frac{1}{2} (g_m r_o)^2 = -\frac{1}{2} A_0^2$$

Homeworkx-due April xx 11p.m.



SEDRA/SMITH Book chapter x problem xx